

CND 121: Introduction to Silicon Process & VLSI

Assignment #: 1

Section #: 16

Submitted by:

Student Name	ID
Aya Reda Osman	V23010305
Hadeer Khaled Abdelmoamen	V23010623
Khlood Rafaat Abdelraouf	V23010199
Aya Ahmed Abdelrahman	V23010284


Submitted to TA: **Mariam Taher Eldin Mohamed Khaled**

Date: 26/9/2023


1. PMOS VI Characteristics

Do the same as in **Lab 01**, but instead of using **NMOS**, use **PMOS** and observe the characteristics of **PMOS**.

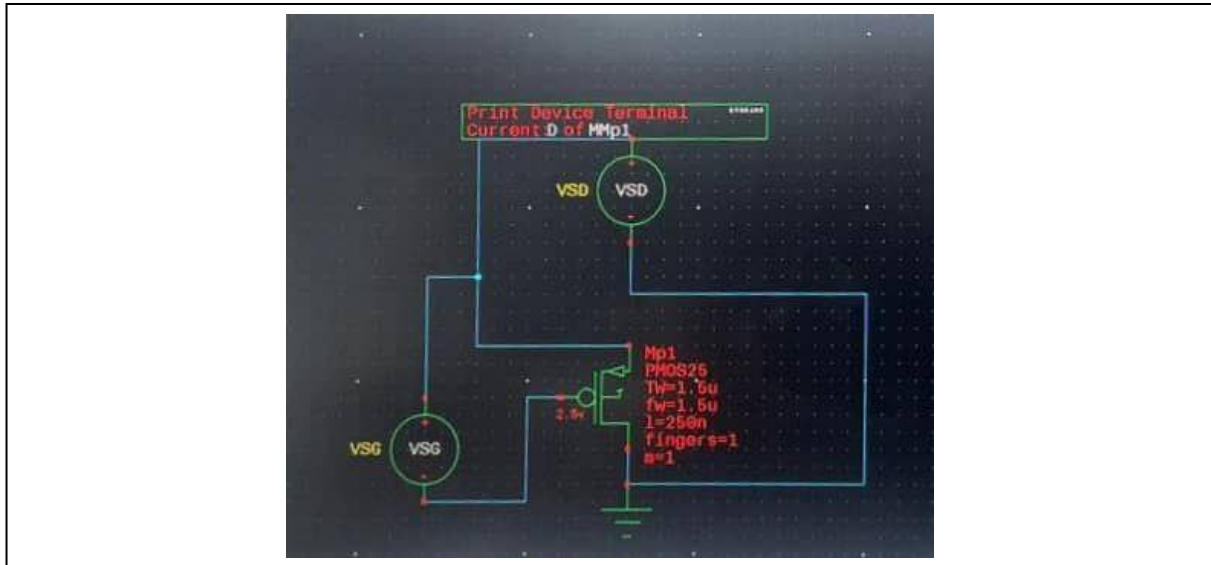- i. Add screenshot from your PMOS schematic:



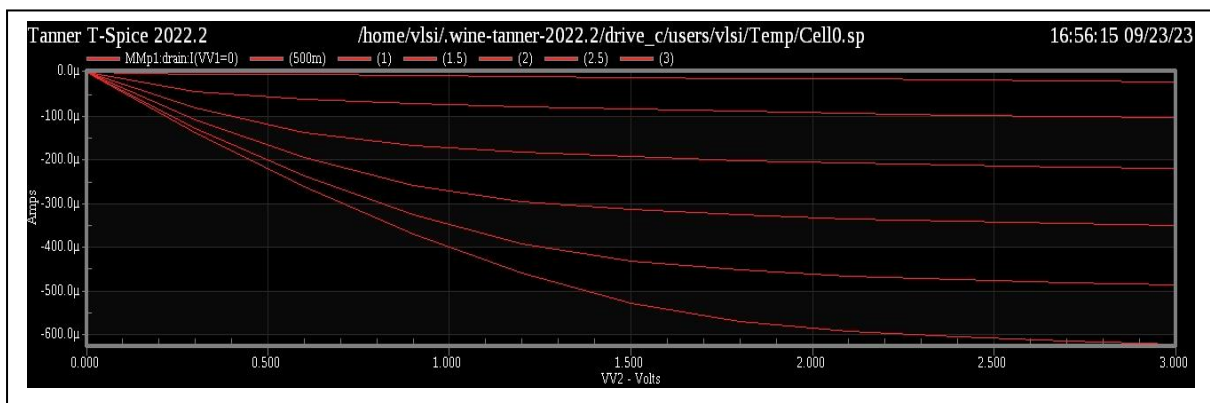- ii. Add screenshot from your waveform viewer showing **PMOS IV Characteristics**:



- iii. **Comment** on the results:

- starting with **VSG=0** the current will be **0Amps** as the pmos transistor will be off and then by increasing **VSG** (negative Value) the current will increase also (negative as **VSG** is negative) and by increasing **VSD** the pmos transistor will be in the triode region until **VSD = VSG - Vth** as then the transistor will enter the saturation region and the current will almost be constant (with some increment due to channel length modulation)