Lab 6: Latch




Objective

The objective of this lab is to go through the full design flow of positive latch, including frontend and backend flow (Design, Simulation, layout, DRC, LVS, Parasitic extraction and post layout simulation).


Frontend Flow

 1. Include libraries


Note: All Libraries used are from technology 2022.




Include all libraries in one step ☺

 

 
You also need to add analog-lib from standard libraries.




Now all done ©

 

 2. Design an Latch from scratch (DON'T use generic gates)




 • First, you should design the transmission gate and create a symbol for it:




NOTE: Don't include global ports while generating symbol.

 
<u>Hint</u>: Use PMOS25x to connect bulk with source, on the other hand use NMOS25x but connect bulk to ground (to avoid errors in LVS because bulk pin by default connected to gnd in layout). **DON'T USE NMOS25 & PMOS25**.



 
• **Second**, you should design the inverter from transistor level (or use the inverter from the previous lab) and create a symbol for it. (Avoid using generic gates)




 NOTE: Don't include global ports while generating symbol.




 • **Finally**, use the TG and inverter symbol to build your latch and create a symbol for it:



 



3. Test your design.

 



<u>Hint</u>: You can use Vpulse for CLK and CLK_bar, and Vbit for D. You can invert Vpulse polarity for for CLK & CLK_bar by **changing High and Low levels**.

4. Simulate

 

 

 

 



Backend Flow

After Finishing your Schematic, now it is time to setup your Layout. The next step is to publish to **SDL** (schematic driven layout).


Important Note for Routing:

- Manhattan routing is a **routing strategy**. You use **one dedicated layer for horizontal tracks** and **another layer for vertical tracks**. No horizontal tracks are allowed on the vertical layer, and no vertical traces are used on the horizontal layer. **Here assume** that all Horizontal connections are metal 1 and all Vertical connections are metal 2.
- To connect metal 1 with metal 2 you will need via Via_M1M2.
- To connect poly with metal 1 you will need via Cnt_poly.
- > To connect poly with metal 2 you will need two vias Cnt_poly & Via_M1M2.

 

 

 1. Generate a layout for inverter and route it:




Routing Hints:

- Connect PMOS gate with NMOS gate using poly.
- Connect PMOS Drain with NMOS Drain using metal 1.
- Connect PMOS Source and Bulk with Vdd using metal 1.
- Connect NMOS Source and Bulk with Gnd using metal 1.
- Convert Z, Vdd and Gnd pins to metal 1 pin (Ctrl + E) and put them over metal 1.
- Convert A pin to poly pin (Ctrl + E) and put it over poly.

Don't forget to run DRC & LVS to validate your inverter ©

 2. Generate a layout for Transmission gate and route it:





Routing Hints:

- Connect PMOS Source with NMOS Drain using metal 1.
- Connect PMOS Drain with NMOS Source using metal 1.
- Connect PMOS Source and Bulk using metal 1.
- Don't connect NMOS Source and Bulk with Gnd (fatal mistake because bulk grounded by default so it will ground source also).
- Convert **Q** and **D** pins to metal **1** pin (Ctrl + E) and put them over metal **1**.
- Convert Clk and Clk_bar pin to poly pin (Ctrl + E) and extend some poly to put over it.

Don't forget to run DRC & LVS to validate your Transmission gate ©

 3. Generate a layout for all latch now and route it:



 


Routing Hints:


- Connect output of inverter 1 to input of Transmission gate 4.
- Connect output of Transmission gate 4 to input of inverter 2.
- Connect output of inverter 3 to input of Transmission gate 5.
- Connect output of Transmission gate 5 to output of Transmission gate 4.
- Connect Clk_bar pin of Transmission gate 4 to Clk pin of Transmission gate 5 (using poly)
 and connect both of them to latch Clk_bar pin after converting it to poly pin (Ctrl + E).
- Connect Clk pin of Transmission gate 4 to Clk_bar pin of Transmission gate 5 (using metal 1 & metal 2) and connect both of them to latch Clk_bar pin after converting it to metal 1 pin (Ctrl + E).
- Connect output of inverter 2 to input of inverter 1.
- Common Vdd for all inverters PMOS.
- Common Gnd for all inverters NMOS.

Calibre Setup

 
Setup Calibre connection **VERY IMPORTANT STEP**:



 
- Note: write MGLS_LISENCE_FILE instead of MGLS_LICENSE_FILE.
- Note: you can find Hostname for Calibre from your tanner location just open it in the terminal of the device.



DRC Setup

 


Cancel the first window appears.

 

Add DRC library from Process file.


"/eda/Mentor/Tanner/TannerTools_v2022.2/Process/Generic_250nm/Rules/Calibre/Generic_250nm DRC.cal"

Use default setting

 

Run DRC


Result view (RVE) window will open

 

Fix all errors & DRC is Done Now ©

LVS SETUP


Run LVS

 


Cancel the first window appears.

Then add LVS library from Process file:

 "/eda/Mentor/Tanner/TannerTools_v2022.2/Process/Generic_250nm/Rules/Calibre/Generic_250nm_LVS.cal"



 


Run LVS

Fix all errors & LVS is Done Now ©

Extraction SETUP


Run **PEX**

Cancel the first window appears.

 



Then add PEX library from Process file.

 "/eda/Mentor/Tanner/TannerTools_v2022.2/Process/Generic_250nm/Rules/Calibre/Generic_250nm xRC.cal"



 If Templates not appears show it from setting >> show pages




 

Post Layout Simulation

Open S-edit

 
Setup >> Preferences >> General >> Calibre



Remove the old cellmap file and add the new path:


"/eda/Mentor/Tanner/TannerTools_v2022.2/Process/Generic_250nm/Rules/Calibre/Generic_250nm.cellmap"

 Press the lamp in the bottom right, import calibre view and press ok



Now right click in your symbol (long click) and choose....

 Netlist >> All instance of this cell >> Choose schematic or mycv_rcc.



Now open your extracted view contains all parasitics and add Vdd & Gnd symbol then save and r-simulate .

